

Reducing the CNOT Count for Clifford+T Circuits on NISQ Architectures

Vlad Gheorghiu², Sarah Meng Li¹, Michele Mosca², and Priyanka Mukhopadhyay².

¹Department of Mathematics and Statistics, Dalhousie University, Halifax NS, Canada

²Institute for Quantum Computing, University of Waterloo, Waterloo ON, Canada

June 22nd 2021

Compilation: Translating a program to a set of elementary quantum gates.


Implementation: Mapping unitary operations to physical architectures.

Connectivity constraint: Applying a multi-qubit gate on admissible qubits.


Clifford+T Circuits

Clifford+T circuits are quantum circuits over the gate set

$$\{CNOT, H, T, S, X, Y, Z\}.$$

 

Basic Gates

 

- CNOT acts on two qubits, *control* c and *target* t :


$$\text{CNOT} |c, t\rangle = |c, c \oplus t\rangle.$$

- X, Y, Z, T, S act on a single qubit:

$$X |t\rangle = |t \oplus 1\rangle, Y |t\rangle = \omega^{4t} |t \oplus 1\rangle, Z |t\rangle = \omega^{4t} |t\rangle, S |t\rangle = \omega^{2t} |t\rangle, T |t\rangle = \omega^t |t\rangle,$$

$c, t \in \mathbb{F}_2$, $\omega = e^{\frac{i\pi}{4}}$, \oplus corresponds to Boolean exclusive-OR.

Basic Gates

 

- CNOT acts on two qubits, *control* c and *target* t :


$$CNOT |c, t\rangle = |c, c \oplus t\rangle .$$

- X , Y , Z , T , S act on a single qubit:

$$X |t\rangle = |t \oplus 1\rangle, Y |t\rangle = \omega^{4t} |t \oplus 1\rangle, Z |t\rangle = \omega^{4t} |t\rangle, S |t\rangle = \omega^{2t} |t\rangle, T |t\rangle = \omega^t |t\rangle,$$

$c, t \in \mathbb{F}_2$, $\omega = e^{\frac{i\pi}{4}}$, \oplus corresponds to Boolean exclusive-OR.

Basic Gates

 

- CNOT acts on two qubits, *control* c and *target* t :

$$CNOT |c, t\rangle = |c, c \oplus t\rangle .$$

- X , Y , Z , T , S act on a single qubit:

$$X |t\rangle = |t \oplus 1\rangle, \quad Y |t\rangle = \omega^{4t} |t \oplus 1\rangle, \quad Z |t\rangle = \omega^{4t} |t\rangle, \quad S |t\rangle = \omega^{2t} |t\rangle, \quad T |t\rangle = \omega^t |t\rangle,$$

$c, t \in \mathbb{F}_2$, $\omega = e^{\frac{i\pi}{4}}$, \oplus corresponds to Boolean exclusive-OR.


Connectivity Graph

Definition

A **graph** is a pair $G = (V_G, E_G)$ where V_G is a set of *vertices* and E_G is a set of pairs $e = (u, v)$ such that $u, v \in V_G$. Each such pair is called an *edge*.

Remark: We are interested in the *simple undirected connected graphs*.

- Simple: there is at most one edge between two distinct vertices and no self-loops.
- Undirected: edges have no direction.

 


Rigetti 16Q-Aspen


Naive Solution

Naively we can insert SWAP operators to move a pair of logical qubits to physical positions admissible for two-qubit operations.

 Example Performing $CNOT_{1,9}$ under the given connectivity constraint.



9-Qubit Square Grid

 


$CNOT_{1,9}$ with SWAPs


Naive Solution

Naively we can insert SWAP operators to move a pair of logical qubits to physical positions admissible for two-qubit operations.

 Example Performing $CNOT_{1,9}$ under the given connectivity constraint.



9-Qubit Square Grid

 

$CNOT_{1,9}$ with SWAPs

Motivation

The diagram shows an equality between two quantum circuit representations. On the left, a swap gate is shown with two input qubits, $|\phi\rangle$ (top) and $|\psi\rangle$ (bottom), and two output qubits, $|\psi\rangle$ (top) and $|\phi\rangle$ (bottom). On the right, the same swap operation is decomposed into three CNOT gates. The top qubit starts with $|\phi\rangle$ and ends with $|\psi\rangle$. The bottom qubit starts with $|\psi\rangle$ and ends with $|\phi\rangle$. The decomposition consists of: 1) a CNOT gate with control on the top qubit and target on the bottom qubit; 2) a CNOT gate with control on the bottom qubit and target on the top qubit; 3) a CNOT gate with control on the top qubit and target on the bottom qubit.

- If the shortest path length between vertices corresponding to c and t in G is ℓ , the naive solution requires about $6(\ell - 1)$ CNOT gates.
- This entails a significant increase in CNOT-count.
- **Can we reduce the CNOT-count while respecting the connectivity constraint?**

We were inspired to use the following techniques.

- Steiner tree problem reduction^{1,2}.

¹Beatrice Nash, Vlad Gheorghiu, and Michele Mosca. “Quantum circuit optimizations for NISQ architectures”. In: *Quantum Science and Technology* 5.2 (2020), p. 025010.

²Aleks Kissinger and Arianne Meijer-van de Griend. “CNOT circuit extraction for topologically-constrained quantum memories”. In: *arXiv preprint arXiv:1904.00633* (2019).

³Ketan N Patel, Igor L Markov, and John P Hayes. “Optimal synthesis of linear reversible circuits”. In: *Quantum Information & Computation* 8.3 (2008), pp. 282–294.

⁴Matthew Amy, Parsiad Azimzadeh, and Michele Mosca. “On the controlled-NOT complexity of controlled-NOT-phase circuits”. In: *Quantum Science and Technology* 4.1 (2018), p. 015002.

We were inspired to use the following techniques.

- Steiner tree problem reduction^{1,2}.
- Linear reversible circuits synthesis³.
- Parity network synthesis⁴.

¹Nash, Gheorghiu, and Mosca, “Quantum circuit optimizations for NISQ architectures”.

²Kissinger and Griend, “CNOT circuit extraction for topologically-constrained quantum memories”.

³Patel, Markov, and Hayes, “Optimal synthesis of linear reversible circuits”.


⁴Amy, Azimzadeh, and Mosca, “On the controlled-NOT complexity of controlled-NOT-phase circuits”.

Steiner Tree


Definition

Given a graph $G = (V_G, E_G)$ and a set of vertices $S \subseteq V_G$, a **Steiner tree** $T = (V_T, E_T)$ is a minimum spanning tree such that $S \subseteq V_T$.

Example G is a simple undirected graph.

 

Terminals: $S = \{1, 6, 7, 11\}$.

 

A solution to the Steiner tree problem on G .
Steiner nodes: $V_T \setminus S = \{4, 5, 8\}$


Slice-and-Build Technique⁵

Slice: Partition the circuit based on the locality of H gates.


Build: Re-synthesize the sliced portions so that connectivity is respected and the CNOT count is reduced.

⁵Vlad Gheorghiu et al. "Reducing the CNOT count for Clifford+ T circuits on NISQ architectures". In: *arXiv preprint arXiv:2011.12191* (2020).

Slice

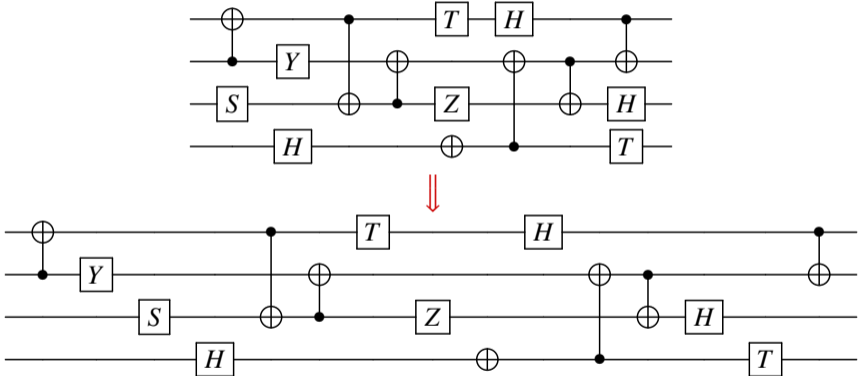

Slice

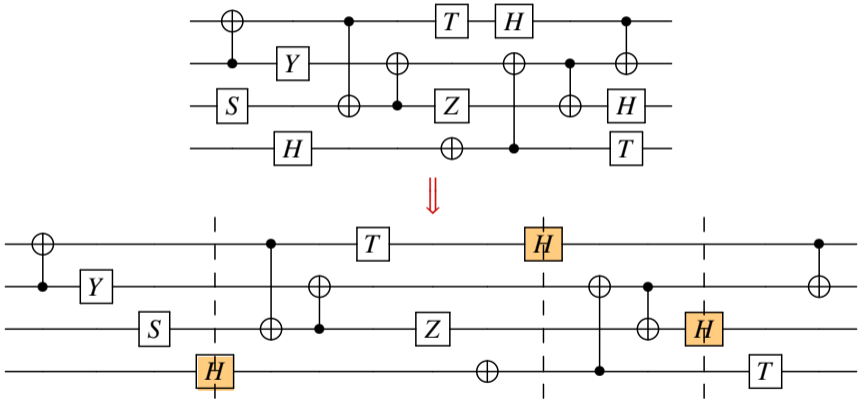

Build

- Each subcircuit is composed of $\mathcal{G}_{ph} = \{CNOT, T, T^\dagger, S, S^\dagger, X, Y, Z\}$.
- Calculate the phase polynomial \mathcal{P} and overall linear transformation A_{slice} .

Build

- Each subcircuit is composed of $\mathcal{G}_{ph} = \{CNOT, T, T^\dagger, S, S^\dagger, X, Y, Z\}$.
- Calculate the phase polynomial \mathcal{P} and overall linear transformation A_{slice} .
- Synthesize a phase polynomial network C_{ph} over \mathcal{G}_{ph} .

Phase Polynomial Network Synthesis

- Each subcircuit is composed of $\mathcal{G}_{ph} = \{CNOT, T, T^\dagger, S, S^\dagger, X, Y, Z\}$.
- Calculate the phase polynomial \mathcal{P} and overall linear transformation A_{slice} .
- Synthesize a phase polynomial network C_{ph} over \mathcal{G}_{ph} .

Phase Polynomial Network Synthesis

- Calculate the overall linear transformation A_{ph} of C_{ph} .

- Each subcircuit is composed of $\mathcal{G}_{ph} = \{CNOT, T, T^\dagger, S, S^\dagger, X, Y, Z\}$.
- Calculate the phase polynomial \mathcal{P} and overall linear transformation \mathbf{A}_{slice} .
- Synthesize a phase polynomial network C_{ph} over \mathcal{G}_{ph} .

Phase Polynomial Network Synthesis

- Calculate the overall linear transformation \mathbf{A}_{ph} of C_{ph} .
- Derive the residual linear transformation $\mathbf{A} = \mathbf{A}_{ph}^{-1} \mathbf{A}_{slice}$.

- Each subcircuit is composed of $\mathcal{G}_{ph} = \{CNOT, T, T^\dagger, S, S^\dagger, X, Y, Z\}$.
- Calculate the phase polynomial \mathcal{P} and overall linear transformation \mathbf{A}_{slice} .
- Synthesize a phase polynomial network C_{ph} over \mathcal{G}_{ph} .

Phase Polynomial Network Synthesis


- Calculate the overall linear transformation \mathbf{A}_{ph} of C_{ph} .
- Derive the residual linear transformation $\mathbf{A} = \mathbf{A}_{ph}^{-1} \mathbf{A}_{slice}$.
- Synthesize a linear reversible circuit C_{lin} over $\{CNOT, X\}$.

Linear Transformation Synthesis

Synthesize Circuits over $\{CNOT, X\}$

For an n -qubit circuit over $\{CNOT, X\}$, we represent the overall linear transformation using an $n \times (n + 1)$ binary matrix.

Example

 


$$\begin{array}{l} |x_2\rangle \\ |x_1 \oplus x_2 \oplus 1\rangle \\ |x_1 \oplus x_2 \oplus x_3 \oplus 1\rangle \\ |x_1 \oplus x_2 \oplus x_4 \oplus 1\rangle \end{array}$$

$$A = \begin{pmatrix} x_1 & x_2 & x_3 & x_4 & b \\ 0 & 1 & 0 & 0 & 0 \\ 1 & 1 & 0 & 0 & 1 \\ 1 & 1 & 1 & 0 & 1 \\ 1 & 1 & 0 & 1 & 1 \end{pmatrix}$$

Synthesize Circuits over $\{CNOT, X\}$

For an n -qubit circuit over $\{CNOT, X\}$, we represent the overall linear transformation using an $n \times (n + 1)$ binary matrix.

Example

 


$$A = \begin{pmatrix} x_1 & x_2 & x_3 & x_4 & b \\ 0 & 1 & 0 & 0 & 0 \\ 1 & 1 & 0 & 0 & 1 \\ 1 & 1 & 1 & 0 & 1 \\ 1 & 1 & 0 & 1 & 1 \end{pmatrix}$$

Synthesize Circuits over $\{CNOT, X\}$

For an n -qubit circuit over $\{CNOT, X\}$, we represent the overall linear transformation using an $n \times (n + 1)$ binary matrix.

Example

 

$$\begin{aligned} &|x_2\rangle \\ &|x_1 \oplus x_2 \oplus 1\rangle \\ &|x_1 \oplus x_2 \oplus x_3 \oplus 1\rangle \\ &|x_1 \oplus x_2 \oplus x_4 \oplus 1\rangle \end{aligned}$$

$$A = \begin{pmatrix} x_1 & x_2 & x_3 & x_4 & b \\ 0 & 1 & 0 & 0 & 0 \\ 1 & 1 & 0 & 0 & 1 \\ 1 & 1 & 1 & 0 & 1 \\ 1 & 1 & 0 & 1 & 1 \end{pmatrix}$$

Linear Transformation Synthesis

Reverse Engineering

- (a) Make $b = 0$ by applying X to corresponding qubits.
- (b) Carry out an analogue of Gaussian elimination.
- (c) Use Steiner tree to incorporate connectivity constraints.


Linear Transformation Synthesis

Reverse Engineering

- (a) Make $b = 0$ by applying X to corresponding qubits.
- (b) Carry out an analogue of Gaussian elimination.
- (c) Use Steiner tree to incorporate connectivity constraints.

 Example Let A be a linear transformation and G be the connectivity graph.

$$A = \begin{bmatrix} 1 & 1 & 0 & 1 & 1 & 0 \\ 0 & 0 & 1 & 1 & 0 & 1 \\ 1 & 0 & 1 & 0 & 1 & 0 \\ 1 & 1 & 0 & 1 & 0 & 0 \\ 1 & 1 & 1 & 1 & 0 & 0 \\ 0 & 1 & 0 & 1 & 0 & 1 \end{bmatrix}$$




Step 1: Reducing A to Upper Triangular Form

Row Operations I

- (a) Starting from the left most column, fix one column at a time.
- (b) Fixing the i th column means applying row operations such that $A_{ii} = 1$ and $A_{ji} = 0$ for every $j > i$.

$$A = \begin{bmatrix} 1 & 1 & 0 & 1 & 1 & 0 \\ 0 & 0 & 1 & 1 & 0 & 1 \\ 1 & 0 & 1 & 0 & 1 & 0 \\ 1 & 1 & 0 & 1 & 0 & 0 \\ 1 & 1 & 1 & 1 & 0 & 0 \\ 0 & 1 & 0 & 1 & 0 & 1 \end{bmatrix}$$

$$T_{1,\{1,3,4,5\}} =$$

 

$$T_1 = \text{1} - \text{2} - \text{3}$$

$$T_2 = \text{3} - \text{4}$$


$$T_3 = \text{4} - \text{5}$$

- The Steiner tree $T_{1,S}$ with pivot 1 and terminals $S = \{1, 3, 4, 5\}$.
- Invoke a sequence of row operations starting from the last sub-tree T_3 .

Step 1: Reducing A to Upper Triangular Form

$$A = \begin{bmatrix} 1 & 1 & 0 & 1 & 1 & 0 \\ 0 & 0 & 1 & 1 & 0 & 1 \\ 1 & 0 & 1 & 0 & 1 & 0 \\ 1 & 1 & 0 & 1 & 0 & 0 \\ 1 & 1 & 1 & 1 & 0 & 0 \\ 0 & 1 & 0 & 1 & 0 & 1 \end{bmatrix}$$

$$T_{1,\{1,3,4,5\}} =$$

 

$$T_1 = \begin{array}{c} \text{1} \text{---} \text{2} \text{---} \text{3} \\ x_1 \oplus x_2 \oplus x_3 \end{array}$$

$$T_2 = \begin{array}{c} \text{3} \text{---} \text{4} \\ x_3 \oplus x_4 \end{array}$$

$$T_3 = \begin{array}{c} \text{4} \text{---} \text{5} \\ x_4 \oplus x_5 \end{array}$$

- Propagate 1 from the root to cancel the 1 at the leaf.
- Cancel the 1s in the intermediate Steiner nodes.
- After traversing subtrees and concatenating CNOTs,

$$\mathcal{Y}_1 = \text{CNOT}_{45} \text{CNOT}_{34} \text{CNOT}_{12} \text{CNOT}_{23} \text{CNOT}_{12}.$$

Step 1: Reducing A to Upper Triangular Form

- When $\text{CNOT}_{j,i}$ is applied, row j is added to row $i \pmod 2$, and row j remains unchanged.
- After a series of row operations, A is reduced to an upper triangular form.

$$A = \begin{bmatrix} \mathbf{1} & 1 & 0 & 1 & 1 & 0 \\ \mathbf{0} & 0 & 1 & 1 & 0 & 1 \\ \mathbf{1} & 0 & 1 & 0 & 1 & 0 \\ \mathbf{1} & 1 & 0 & 1 & 0 & 0 \\ \mathbf{1} & 1 & 1 & 1 & 0 & 0 \\ \mathbf{0} & 1 & 0 & 1 & 0 & 1 \end{bmatrix} \xrightarrow{y_1} A = \begin{bmatrix} \mathbf{1} & 1 & 0 & 1 & 1 & 0 \\ \mathbf{0} & 0 & 1 & 1 & 0 & 1 \\ \mathbf{0} & 1 & 0 & 0 & 0 & 1 \\ \mathbf{0} & 1 & 1 & 1 & 1 & 0 \\ \mathbf{0} & 0 & 1 & 0 & 0 & 0 \\ \mathbf{0} & 1 & 0 & 1 & 0 & 1 \end{bmatrix} \xrightarrow{y_2} \dots \xrightarrow{y_6} A = \begin{bmatrix} \mathbf{1} & 1 & 0 & 1 & 1 & 0 \\ \mathbf{0} & 1 & 1 & 1 & 0 & 0 \\ \mathbf{0} & 0 & 1 & 1 & 0 & 1 \\ \mathbf{0} & 0 & 0 & 1 & 0 & 1 \\ \mathbf{0} & 0 & 0 & 0 & 1 & 0 \\ \mathbf{0} & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$


Step 2: Reducing A^T to Identity

Row Operations II

- (a) Starting from the left most column, fix one column at a time.
- (b) Fixing the i th column means applying row operations such that $A_{ii} = 1$ and $A_{ji} = 0$ for every $j > i$.

$$A = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & 0 \\ 1 & 1 & 1 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & 1 & 0 & 1 \end{bmatrix}$$

$$T_{1,\{1,2,4,5\}} =$$

 

$$T_1 = \text{①} - \text{②}$$

$x_1 \oplus x_2$

$$T_2 = \text{②} - \text{⑤}$$

$x_2 \oplus x_5$

$$T_3 = \text{⑤} - \text{④}$$

$x_5 \oplus x_4$

- A row should be XORed with a row of lower index.
- If not, apply a correction procedure after traversing all sub-trees.

Synthesize Circuits over $\{CNOT, X, T\}$

- Consider circuits over the gate set

$$\mathcal{G}_{ph} = \{CNOT, X, T, T^\dagger, S, S^\dagger, Y, Z\}.$$

- $CNOT |x, y\rangle = |x, x \oplus y\rangle$, $T |x\rangle = \omega^x |x\rangle$, where $\omega = e^{\frac{i\pi}{4}}$ and $x, y \in \mathbb{F}_2$.


Synthesize Circuits over $\{CNOT, X, T\}$

- Consider circuits over the gate set

$$\mathcal{G}_{ph} = \{CNOT, X, T, T^\dagger, S, S^\dagger, Y, Z\}.$$

- $CNOT |x, y\rangle = |x, x \oplus y\rangle$, $T |x\rangle = \omega^x |x\rangle$, where $\omega = e^{\frac{i\pi}{4}}$ and $x, y \in \mathbb{F}_2$.

Example

 


Synthesize Circuits over $\{CNOT, X, T\}$

- Consider circuits over the gate set


$$\mathcal{G}_{ph} = \{CNOT, X, T, T^\dagger, S, S^\dagger, Y, Z\}.$$

- $CNOT |x, y\rangle = |x, x \oplus y\rangle$, $T |x\rangle = \omega^x |x\rangle$, where $\omega = e^{\frac{i\pi}{4}}$ and $x, y \in \mathbb{F}_2$.

Example

 


 Phase Polynomial Network [Amy et al., 2014]




- A **representation** of linear reversible functions: $\mathbf{A} = \begin{bmatrix} 0 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ 1 & 1 & 1 & 1 \\ 1 & 1 & 0 & 1 \end{bmatrix}$.

 Phase Polynomial Network [Amy et al., 2014]



- A **representation** of linear reversible functions: $\mathbf{A} = \begin{bmatrix} 0 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ 1 & 1 & 1 & 1 \\ 1 & 1 & 0 & 1 \end{bmatrix}$.
- A **phase polynomial set**: $\mathcal{P} = \{(1, x_1), (1, x_3 \oplus x_4), (1, x_3), (1, x_1 \oplus x_2 \oplus x_3 \oplus x_4), (7, x_2)\}$.

 Phase Polynomial Network [Amy et al., 2014]



- A **representation** of linear reversible functions: $\mathbf{A} = \begin{bmatrix} 0 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ 1 & 1 & 1 & 1 \\ 1 & 1 & 0 & 1 \end{bmatrix}$.
- A **phase polynomial set**: $\mathcal{P} = \{(1, x_1), (1, x_3 \oplus x_4), (1, x_3), (1, x_1 \oplus x_2 \oplus x_3 \oplus x_4), (7, x_2)\}$.
- A **phase polynomial network**: a 4-qubit circuit over $\{CNOT, X, T\}$ such that for every $(c, f) \in \mathcal{P}$, f appears before a gate in $\{T, T^\dagger, S, S^\dagger, Y, Z\}$.


Phase Polynomial Network Synthesis

- (a) Calculate a parity network matrix M to represent \mathcal{P} .
- (b) Construct Steiner tree to impose connectivity constraints.
- (c) Synthesize a circuit over $\{CNOT, X\}$ that realizes each column in M .
- (d) Apply $\{T, T^\dagger, S, S^\dagger, Y, Z\}$ depending on the coefficients of the parity terms $(c, f) \in \mathcal{P}$.

Columns Represent Parity Term

$$\mathcal{P} = \{(1, 1 \oplus x_1 \oplus x_4 \oplus x_5), (2, x_2 \oplus x_3 \oplus x_5 \oplus x_6), (4, 1 \oplus x_4 \oplus x_5 \oplus x_6), (4, 1 \oplus x_1 \oplus x_2 \oplus x_6), (6, 1 \oplus x_1 \oplus x_2 \oplus x_3), (7, 1 \oplus x_1 \oplus x_2 \oplus x_4 \oplus x_6), (1, x_2 \oplus x_4 \oplus x_5)\}$$
 
$$M = \begin{bmatrix} \underline{p_1} & \underline{p_2} & \underline{p_3} & \underline{p_4} & \underline{p_5} & \underline{p_6} & \underline{p_7} \\ 1 & 0 & 0 & 1 & 1 & 1 & 0 \\ 0 & 1 & 0 & 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 0 & 1 & 0 & 0 \\ 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 1 & 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 1 & 1 & 0 & 1 & 0 \\ 1 & 0 & 1 & 1 & 1 & 1 & 0 \\ 1 & 2 & 4 & 4 & 6 & 7 & 1 \end{bmatrix}$$




The parity matrix $M_{8 \times 7}$ and connectivity graph G .

Top Six Rows Encode Parity

$$\mathcal{P} = \{(1, 1 \oplus x_1 \oplus x_4 \oplus x_5), (2, x_2 \oplus x_3 \oplus x_5 \oplus x_6), (4, 1 \oplus x_4 \oplus x_5 \oplus x_6), (4, 1 \oplus x_1 \oplus x_2 \oplus x_6), (6, 1 \oplus x_1 \oplus x_2 \oplus x_3), (7, 1 \oplus x_1 \oplus x_2 \oplus x_4 \oplus x_6), (1, x_2 \oplus x_4 \oplus x_5)\}$$
 
$$M = \begin{bmatrix} \underline{p_1} & \underline{p_2} & \underline{p_3} & \underline{p_4} & \underline{p_5} & \underline{p_6} & \underline{p_7} \\ 1 & 0 & 0 & 1 & 1 & 1 & 0 \\ 0 & 1 & 0 & 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 0 & 1 & 0 & 0 \\ 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 0 & 1 & 1 & 0 & 0 & 0 & 1 \\ 1 & 1 & 1 & 1 & 0 & 1 & 0 \\ 1 & 0 & 1 & 1 & 1 & 1 & 0 \\ 1 & 2 & 4 & 4 & 6 & 7 & 1 \end{bmatrix}$$




The parity matrix $M_{8 \times 7}$ and connectivity graph G .

The 7th Row Encodes Bit Flip

$$\mathcal{P} = \{(1, 1 \oplus x_1 \oplus x_4 \oplus x_5), (2, x_2 \oplus x_3 \oplus x_5 \oplus x_6), (4, 1 \oplus x_4 \oplus x_5 \oplus x_6), (4, 1 \oplus x_1 \oplus x_2 \oplus x_6), (6, 1 \oplus x_1 \oplus x_2 \oplus x_3), (7, 1 \oplus x_1 \oplus x_2 \oplus x_4 \oplus x_6), (1, x_2 \oplus x_4 \oplus x_5)\}$$

$$M = \begin{bmatrix} \underline{p_1} & \underline{p_2} & \underline{p_3} & \underline{p_4} & \underline{p_5} & \underline{p_6} & \underline{p_7} \\ 1 & 0 & 0 & 1 & 1 & 1 & 0 \\ 0 & 1 & 0 & 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 0 & 1 & 0 & 0 \\ 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 1 & 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 1 & 1 & 0 & 1 & 0 \\ \mathbf{1} & \mathbf{0} & \mathbf{1} & \mathbf{1} & \mathbf{1} & \mathbf{1} & \mathbf{0} \\ 1 & 2 & 4 & 4 & 6 & 7 & 1 \end{bmatrix}$$

 


The parity matrix $M_{8 \times 7}$ and connectivity graph G .

The Last Row Stores Coefficients

$$\mathcal{P} = \{(1, 1 \oplus x_1 \oplus x_4 \oplus x_5), (2, x_2 \oplus x_3 \oplus x_5 \oplus x_6), (4, 1 \oplus x_4 \oplus x_5 \oplus x_6), (4, 1 \oplus x_1 \oplus x_2 \oplus x_6), (6, 1 \oplus x_1 \oplus x_2 \oplus x_3), (7, 1 \oplus x_1 \oplus x_2 \oplus x_4 \oplus x_6), (1, x_2 \oplus x_4 \oplus x_5)\}$$

 
$$M = \begin{bmatrix} \underline{p_1} & \underline{p_2} & \underline{p_3} & \underline{p_4} & \underline{p_5} & \underline{p_6} & \underline{p_7} \\ 1 & 0 & 0 & 1 & 1 & 1 & 0 \\ 0 & 1 & 0 & 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 0 & 1 & 0 & 0 \\ 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 1 & 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 1 & 1 & 0 & 1 & 0 \\ 1 & 0 & 1 & 1 & 1 & 1 & 0 \\ 1 & 2 & 4 & 4 & 6 & 7 & 1 \end{bmatrix}$$




The parity matrix $M_{8 \times 7}$ and connectivity graph G .

Implementation

 We simulated benchmarks and random circuits on five popular architectures such as (1) 9-qubit square grid, (2) Rigetti 16-qubit Aspen, (3) 16-qubit square grid, (4) 16-qubit IBM QX5, and (5) 20-qubit IBM Tokyo.



(2) Rigetti 16Q-Aspen

 

(3) 16q-Square Grid

Compare the Increase in CNOT-Count

Architecture	#Qubits	Initial count	SWAP-template Count	Slide-and-Build	
				Count	Time
9q-square	9	3	560%	0%	0.184s
		5	612%	146%	0.146s
		10	594%	105%	0.167s
		20	546%	176%	0.2s
		30	596%	185%	0.233s
16q-square	16	4	1050%	238%	0.23s
		8	840%	146%	0.27s
		16	818%	158%	0.43s
		32	853%	341%	0.41s
		64	893%	221%	0.49s
		128	859%	211%	0.57s
		256	897%	238%	0.72s
rigetti-16q-aspen	16	4	1680%	355%	0.23s
		8	1740%	253%	0.396s
		16	1620%	351%	0.47s
		32	1794%	470%	0.48s
		64	1755%	399%	0.66s
		128	1761%	368%	0.58s
		256	1757%	411%	0.61s

Compare the Increase in CNOT Count

Architecture	#Qubits	Initial count	SWAP-template Count	Slide-and-Build	
				Count	Time
9q-square	9	3	560%	0%	0.184s
		5	612%	146%	0.146s
		10	594%	105%	0.167s
		20	546%	176%	0.2s
		30	596%	185%	0.233s
16q-square	16	4	1050%	238%	0.23s
		8	840%	146%	0.27s
		16	818%	158%	0.43s
		32	853%	341%	0.41s
		64	893%	221%	0.49s
		128	859%	211%	0.57s
		256	897%	238%	0.72s
rigetti-16q-aspen	16	4	1680%	355%	0.23s
		8	1740%	253%	0.396s
		16	1620%	351%	0.47s
		32	1794%	470%	0.48s
		64	1755%	399%	0.66s
		128	1761%	368%	0.58s
		256	1757%	411%	0.61s

Compare the Increase in CNOT Count

Architecture	#Qubits	Initial count	SWAP-template Count	Slide-and-Build	
				Count	Time
ibm-qx5	16	4	1260%	173%	0.38s
		8	1035%	295%	0.36s
		16	1043%	283%	0.41s
		32	1179%	398%	0.42s
		64	1131%	339%	0.45s
		128	1111%	345%	0.575s
		256	1141%	380%	0.73s
ibm-q20-tokyo	20	4	525%	128%	0.186s
		8	555%	275%	0.295s
		16	570%	88%	0.37s
		32	501%	154%	0.55s
		64	543%	137%	0.54s
		128	540%	141%	0.645s
		256	535%	125%	0.72s

Conclusion

- We designed a heuristic algorithm that reduces the CNOT count in Clifford+T circuits while accounting for the connectivity constraints.
- It's possible to improve the results by optimizing the initial mapping from logical qubits to physical qubits.
- Moving forward, we would like to rigorously benchmark against other compilers such as tket by CQC and Qiskit by IBM.




Thank you!

Avoid Disturbing 0s' in Upper Triangle

- A node (row) should be XORed with a row with a higher-index.
- If not, apply a correction procedure after traversing all sub-trees.

Example Work with a violation in T_3 .

 


- Take the shortest path from 5 to 4 and apply the same traversals: CNOT_{54}
- The parity at 4 becomes $x'_4 \oplus x'_5 = (x_5 \oplus x_4) \oplus (x_2 \oplus x_5) = x_4 \oplus x_2$.

Columns Represent Parity Term

$$\mathcal{P} = \{(1, 1 \oplus x_1 \oplus x_4 \oplus x_5), (2, x_2 \oplus x_3 \oplus x_5 \oplus x_6), (4, 1 \oplus x_4 \oplus x_5 \oplus x_6), (4, 1 \oplus x_1 \oplus x_2 \oplus x_6), (6, 1 \oplus x_1 \oplus x_2 \oplus x_3), (7, 1 \oplus x_1 \oplus x_2 \oplus x_4 \oplus x_6), (1, x_2 \oplus x_4 \oplus x_5)\}$$
 
$$P = \begin{bmatrix} \underline{p_1} & \underline{p_2} & \underline{p_3} & \underline{p_4} & \underline{p_5} & \underline{p_6} & \underline{p_7} \\ 1 & 0 & 0 & 1 & 1 & 1 & 0 \\ 0 & 1 & 0 & 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 0 & 1 & 0 & 0 \\ 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 1 & 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 1 & 1 & 0 & 1 & 0 \\ 1 & 0 & 1 & 1 & 1 & 1 & 0 \\ 1 & 2 & 4 & 4 & 6 & 7 & 1 \end{bmatrix}$$




The parity matrix $P_{8 \times 7}$ and connectivity graph G .

Top Six Rows Encode Parity

$$\mathcal{P} = \{(1, 1 \oplus x_1 \oplus x_4 \oplus x_5), (2, x_2 \oplus x_3 \oplus x_5 \oplus x_6), (4, 1 \oplus x_4 \oplus x_5 \oplus x_6), (4, 1 \oplus x_1 \oplus x_2 \oplus x_6), (6, 1 \oplus x_1 \oplus x_2 \oplus x_3), (7, 1 \oplus x_1 \oplus x_2 \oplus x_4 \oplus x_6), (1, x_2 \oplus x_4 \oplus x_5)\}$$
 
$$P = \begin{bmatrix} \underline{p_1} & \underline{p_2} & \underline{p_3} & \underline{p_4} & \underline{p_5} & \underline{p_6} & \underline{p_7} \\ 1 & 0 & 0 & 1 & 1 & 1 & 0 \\ 0 & 1 & 0 & 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 0 & 1 & 0 & 0 \\ 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 1 & 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 1 & 1 & 0 & 1 & 0 \\ 1 & 0 & 1 & 1 & 1 & 1 & 0 \\ 1 & 2 & 4 & 4 & 6 & 7 & 1 \end{bmatrix}$$




The parity matrix $P_{8 \times 7}$ and connectivity graph G .

The 7th Row Encodes Bit Flip

$$\mathcal{P} = \{(1, 1 \oplus x_1 \oplus x_4 \oplus x_5), (2, x_2 \oplus x_3 \oplus x_5 \oplus x_6), (4, 1 \oplus x_4 \oplus x_5 \oplus x_6), (4, 1 \oplus x_1 \oplus x_2 \oplus x_6), (6, 1 \oplus x_1 \oplus x_2 \oplus x_3), (7, 1 \oplus x_1 \oplus x_2 \oplus x_4 \oplus x_6), (1, x_2 \oplus x_4 \oplus x_5)\}$$

$$P = \begin{bmatrix} \underline{p_1} & \underline{p_2} & \underline{p_3} & \underline{p_4} & \underline{p_5} & \underline{p_6} & \underline{p_7} \\ 1 & 0 & 0 & 1 & 1 & 1 & 0 \\ 0 & 1 & 0 & 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 0 & 1 & 0 & 0 \\ 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 1 & 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 1 & 1 & 0 & 1 & 0 \\ \mathbf{1} & \mathbf{0} & \mathbf{1} & \mathbf{1} & \mathbf{1} & \mathbf{1} & \mathbf{0} \\ 1 & 2 & 4 & 4 & 6 & 7 & 1 \end{bmatrix}$$

 


The parity matrix $P_{8 \times 7}$ and connectivity graph G .

The Last Row Stores Coefficients

$$\mathcal{P} = \{(1, 1 \oplus x_1 \oplus x_4 \oplus x_5), (2, x_2 \oplus x_3 \oplus x_5 \oplus x_6), (4, 1 \oplus x_4 \oplus x_5 \oplus x_6), (4, 1 \oplus x_1 \oplus x_2 \oplus x_6), (6, 1 \oplus x_1 \oplus x_2 \oplus x_3), (7, 1 \oplus x_1 \oplus x_2 \oplus x_4 \oplus x_6), (1, x_2 \oplus x_4 \oplus x_5)\}$$
 
$$P = \begin{bmatrix} \underline{p_1} & \underline{p_2} & \underline{p_3} & \underline{p_4} & \underline{p_5} & \underline{p_6} & \underline{p_7} \\ 1 & 0 & 0 & 1 & 1 & 1 & 0 \\ 0 & 1 & 0 & 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 0 & 1 & 0 & 0 \\ 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 1 & 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 1 & 1 & 0 & 1 & 0 \\ 1 & 0 & 1 & 1 & 1 & 1 & 0 \\ 1 & 2 & 4 & 4 & 6 & 7 & 1 \end{bmatrix}$$



The parity matrix $P_{8 \times 7}$ and connectivity graph G .

PHASE-NW-SYNTH Algorithm Snapshot

- Ignore the last two rows of P , let $B = \{p'_1, p'_2, p'_3, p'_4, p'_5, p'_6, p'_7\}$, \mathcal{K} be an empty stack, and $I = [6]$.
- Cycle through the set of n -bit strings and apply corresponding $CNOT$ gates at each iteration.
- Whenever a column has a single 1, it implies that the corresponding parity has been realized.

Example After the 4th iteration, we have

$$B^{(4)} = \begin{bmatrix} \frac{p'_1}{1} & \frac{p'_2}{0} & \frac{p'_3}{0} & \frac{p'_4}{1} & \frac{p'_5}{1} & \frac{p'_6}{1} & \frac{p'_7}{0} \\ 0 & 1 & 0 & 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 0 & 1 & 0 & 0 \\ 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 0 & 1 & 0 & 0 & 0 & 1 & 0 \\ 1 & 0 & 0 & 1 & 0 & 1 & 1 \end{bmatrix}$$

PHASE-NW-SYNTH Algorithm Snapshot

- Whenever a column has a single 1, it implies that the corresponding parity has been realized.
- Remove these columns from the remaining parities.
- Place the gate X if parity realized on circuit is $1 \oplus f$ for some $(c, f) \in \mathcal{P}$. We can also place a gate in $\{T, T^\dagger, S, S^\dagger, Z, Y\}$ corresponding to the value of the coefficient c .

Example The partial circuit obtained after applying a sequence of gates from iteration 4.

$$B^{(4)} = \begin{bmatrix} \underline{p'_1} & \underline{p'_2} & \underline{p'_3} & \underline{p'_4} & \underline{p'_5} & \underline{p'_6} & \underline{p'_7} \\ 1 & 0 & 0 & 1 & 1 & 1 & 0 \\ 0 & 1 & 0 & 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 0 & 1 & 0 & 0 \\ 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 0 & 1 & 0 & 0 & 0 & 1 & 0 \\ 1 & 0 & 0 & 1 & 0 & 1 & 1 \end{bmatrix}$$

